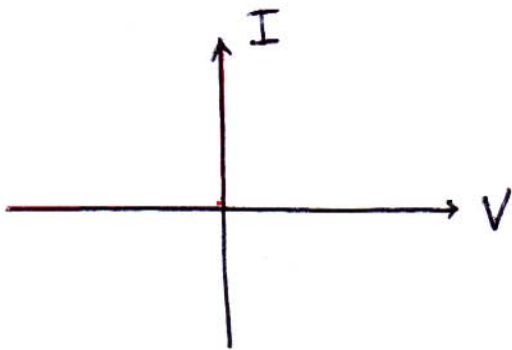


## Lecture 13


Diodes

- 2 terminal

1) ideal diode



2) real diode

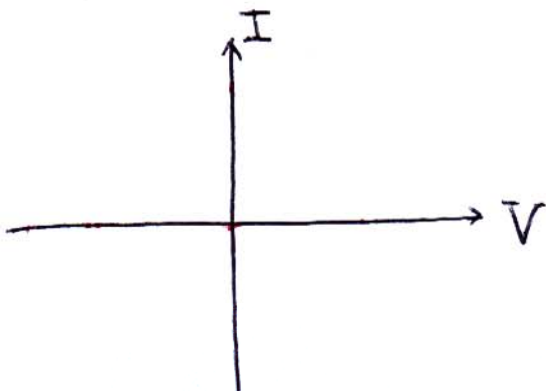

Shockley equation

$$I = I_0 \left( e^{\frac{V}{V_T^*}} - 1 \right)$$

 $I_0$ - $V_T^*$ -

3) diode resistance

(2)

$$R_D = \frac{V}{I} =$$

$$r_d = \frac{dV}{dI} =$$

4) modes of operation

V	I (mA)	$R_D (\Omega)$	$r_d (\Omega)$
0.1			
0.2			
0.3			
0.4			
0.5			
0.6			
0.7			
0.8			
0.9			
1.0			

## 5) max ratings

③


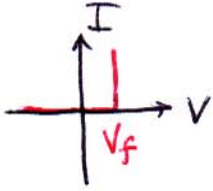
forward  $I_{max}$  (DC)  
 $V_{br}$

Power dissipation on a diode  $P = I \cdot V$


For fixed  $I$ ,  $\frac{dV}{dT} \approx -2 \text{ mV}/^\circ\text{C}$

E.g. fixed voltage bias:
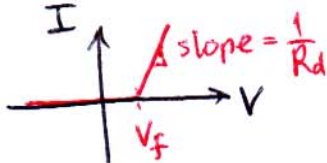
## Diode circuit analysis

ideal diode   $\rightarrow$  approximate model 

$\rightarrow$  approximate resistive model  $\rightarrow$  Shockley eqn.



## Diode types

- signal: fast, small  $I$
- power (rectifier): large  $I$

- Zener: const  $V_{br} = V_z$
- LED: GaAs, InP  $V_f \approx 1.5-2 \text{ V}$

# Diode applications


④

① rectifiers

High voltage lines:

To step down high volt:

DC power supply

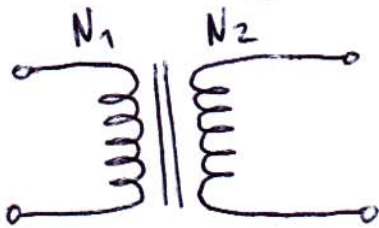

i) transformer

Lecture 14





Diode Applications (contd.)

① rectifiers

recall filter capacitor

ripple:  $\frac{dV}{dt} = \frac{I}{C}$ ,


full wave rectifier

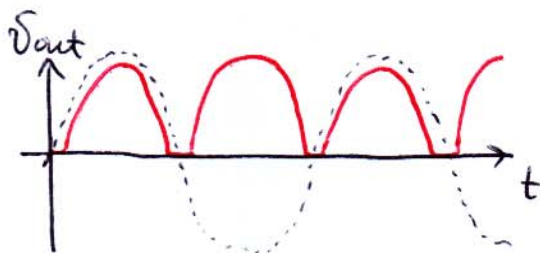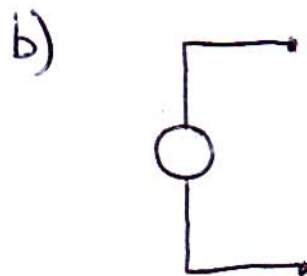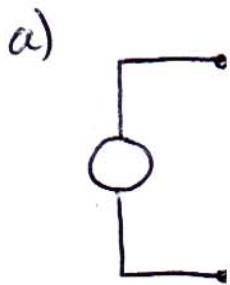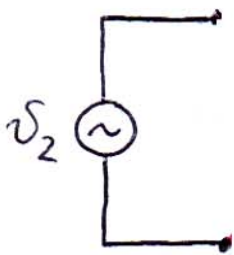




Pros: -  
-

## ② Zener voltage reference



②

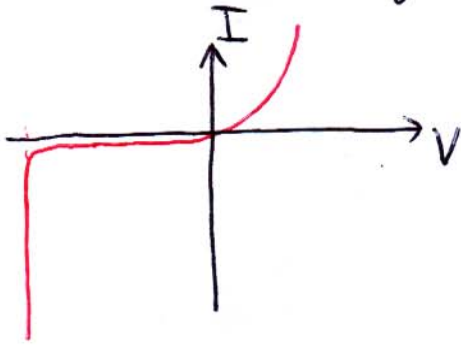


## ③ Clipping circuit

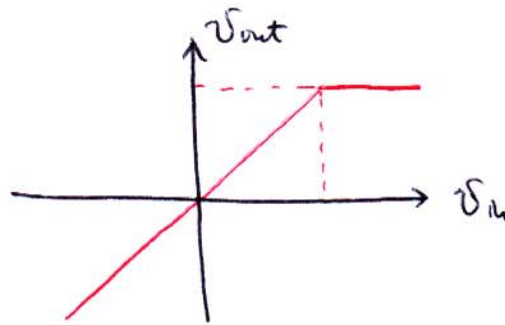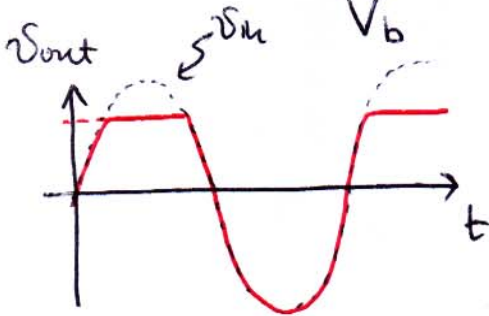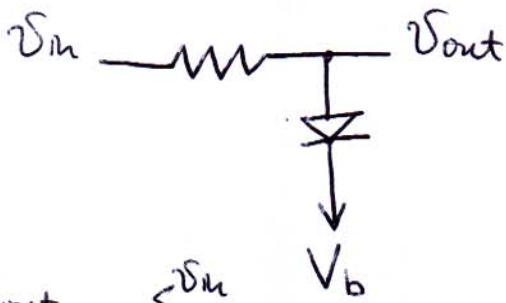


## ④ Pickoff circuit

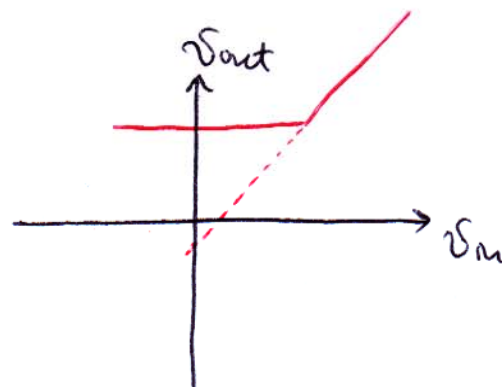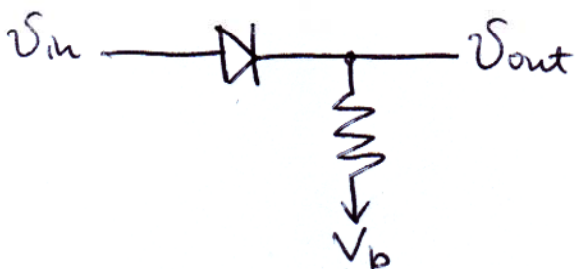

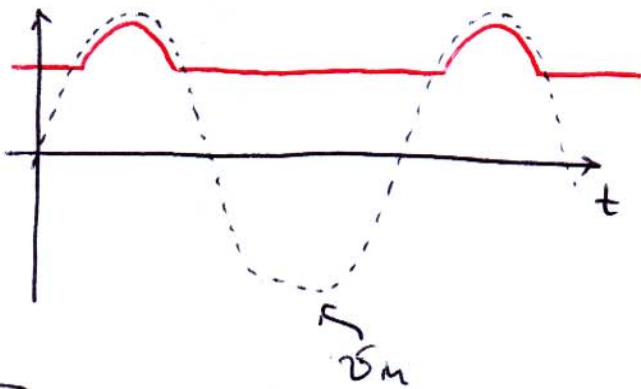


⑤ Voltage doubler

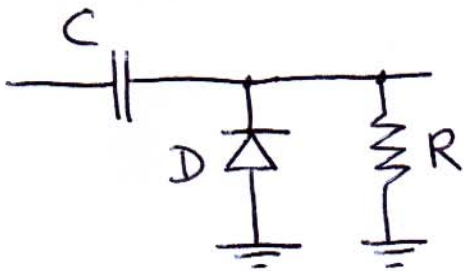



$$v_m - v_c < -V_f$$

$$v_m - v_c > -V_f$$

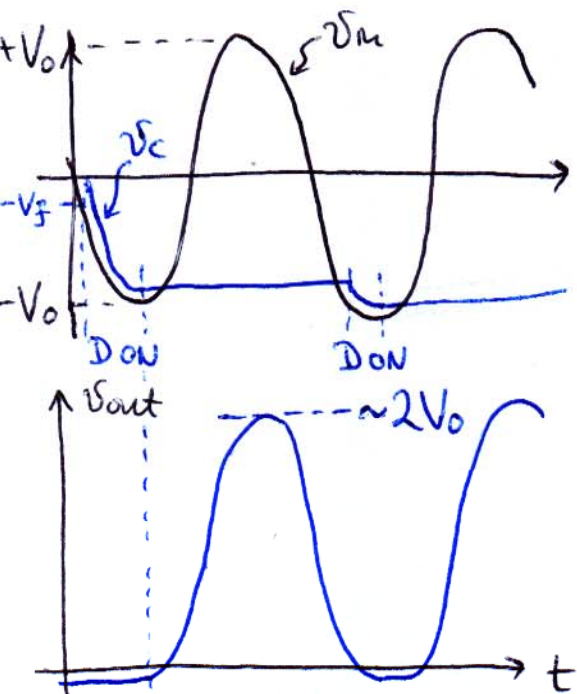


# ⑥ DC restoration circuit

④

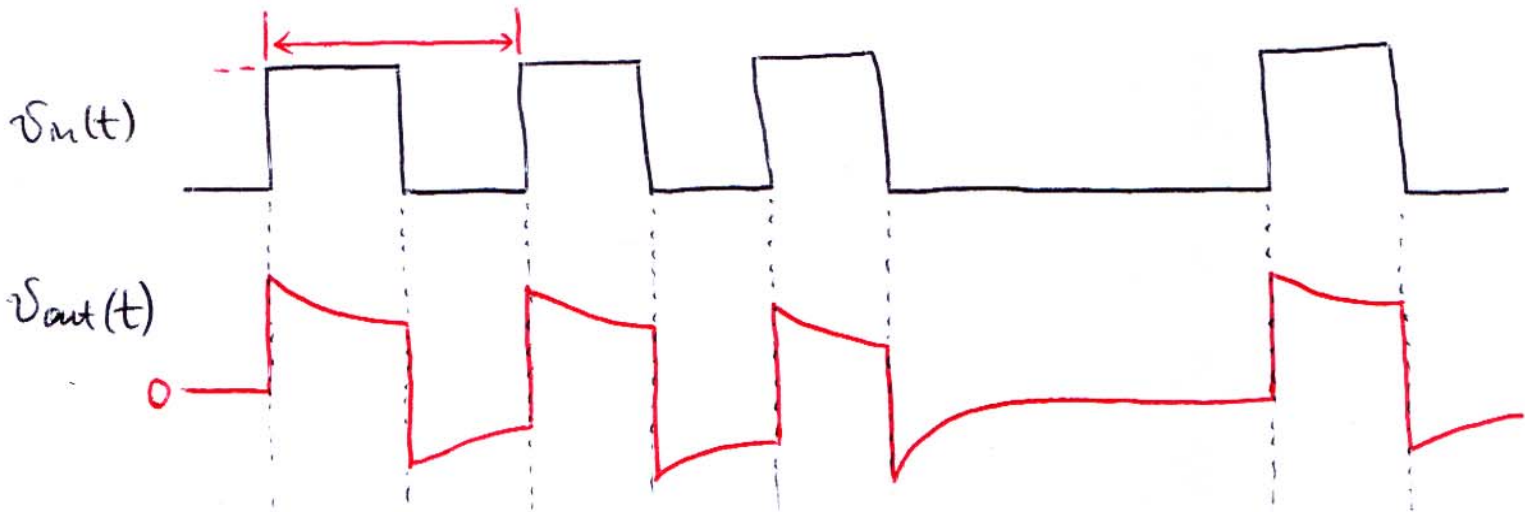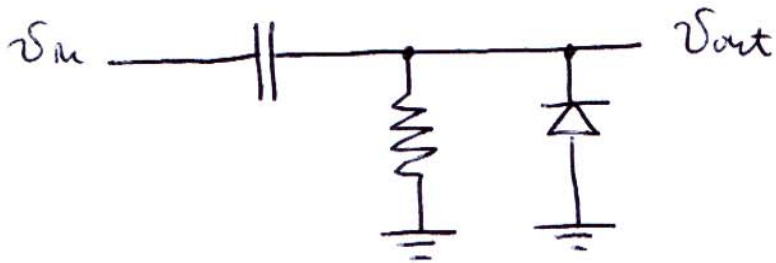

Problem :


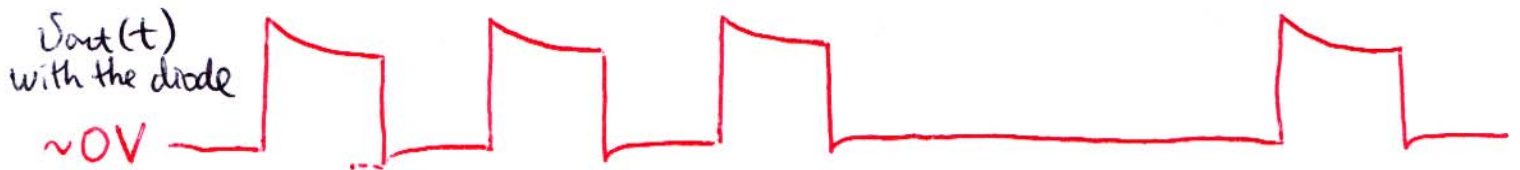





## Lecture 15

Diode applications (contd.)

## ⑦ Pulse stretcher

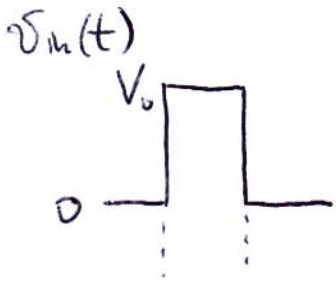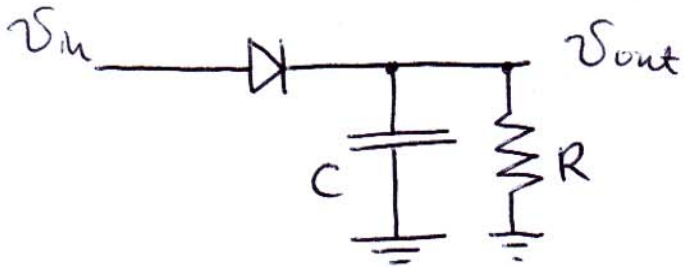

## ⑧ Log amplifier

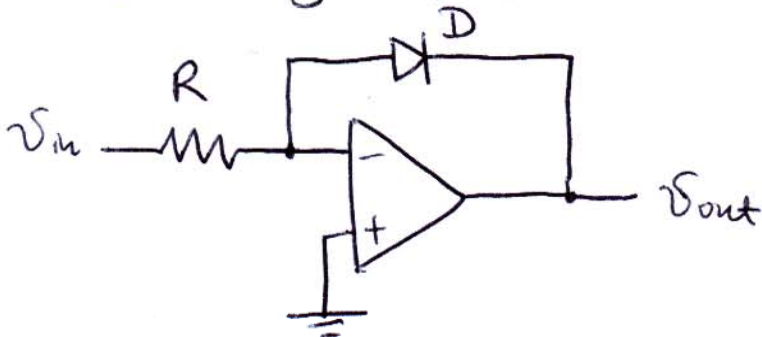

- use to

- use to

### ⑨ Anti-log amplifier

Diode :

Transistor :  
\_

# Bipolar junction transistor


③

2 types

arrow on emitter :


npn  $\leftrightarrow$  pnp

npn

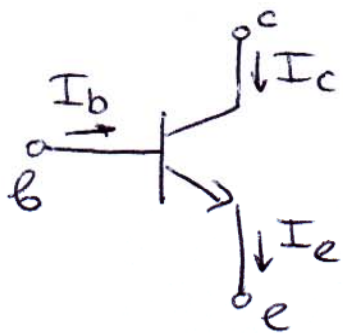

KCL :  $I_e = I_b + I_c$

Typical values:

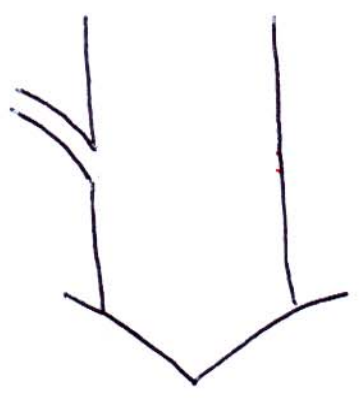

$I_c$  is controlled by  $I_b$   
 $\Rightarrow$  transistor in normal operation

N.B. transistor

