

Recap

Lecture 23

• Magnetic field energy:

- Energy stored in an inductor: $U_B = \frac{1}{2} L i^2$

- Energy density of a magnetic field: $u_B = \frac{1}{2} \frac{B^2}{\mu_0}$

• Alternating current (ac):

- $\mathcal{E}(t) = \mathcal{E}_{\max} \sin(2\pi f t)$



- $i_R(t) = \underbrace{i_{\max}}_{= \mathcal{E}_{\max} / R} \sin(2\pi f t)$

- average power dissipated in resistor:

$$P_{\text{avg}} = \left(\frac{i_{\max}}{\sqrt{2}} \right)^2 R = i_{R(\text{rms})}^2 R = i_{R(\text{rms})} \Delta V_{R(\text{rms})}$$


- RMS values:
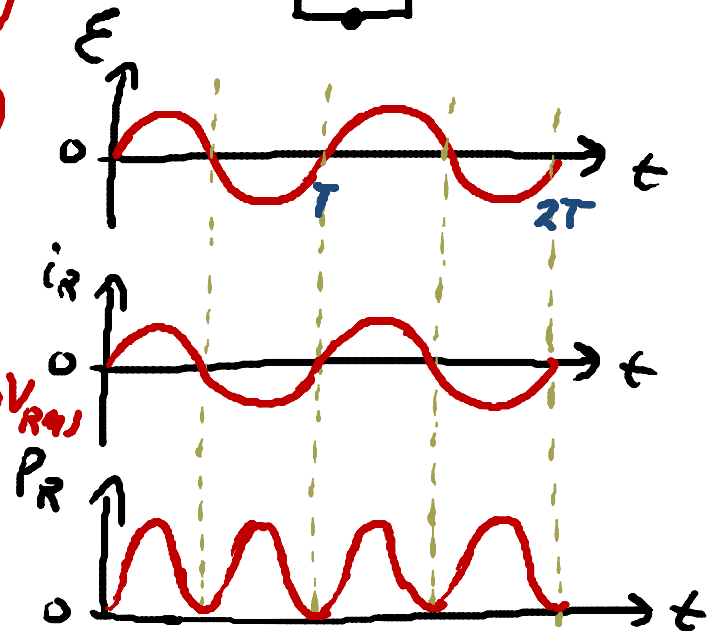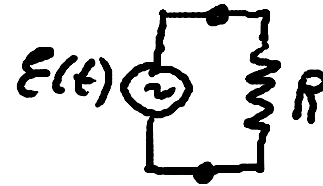
$$i_{R(\text{rms})} = \frac{i_{\max}}{\sqrt{2}} \quad \Delta V_{R(\text{rms})} = \frac{\Delta V_{\max}}{\sqrt{2}}$$




Today:

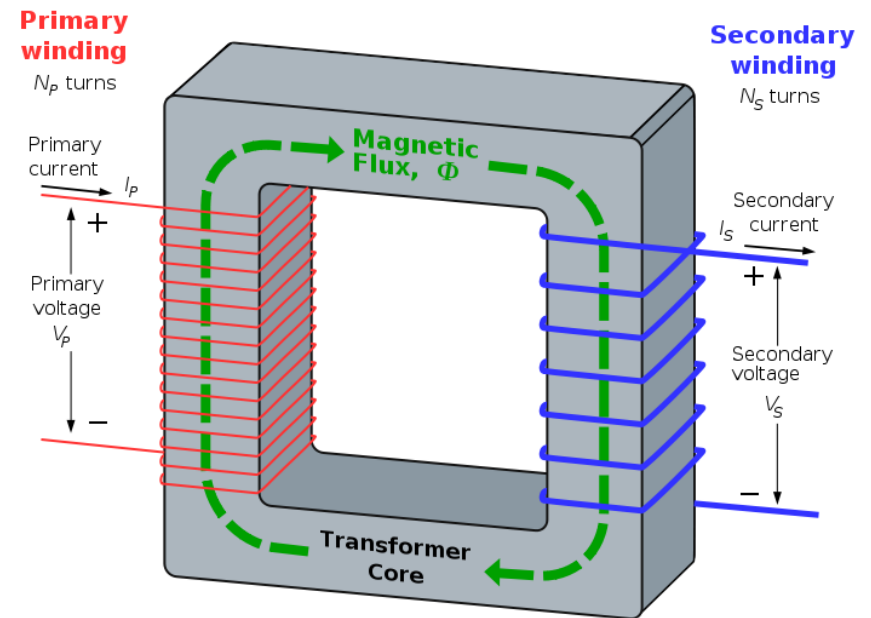- Alternating current and power
 - Transformers
- Ideal LC circuit
- RLC circuit: damping and driven




Transformer:

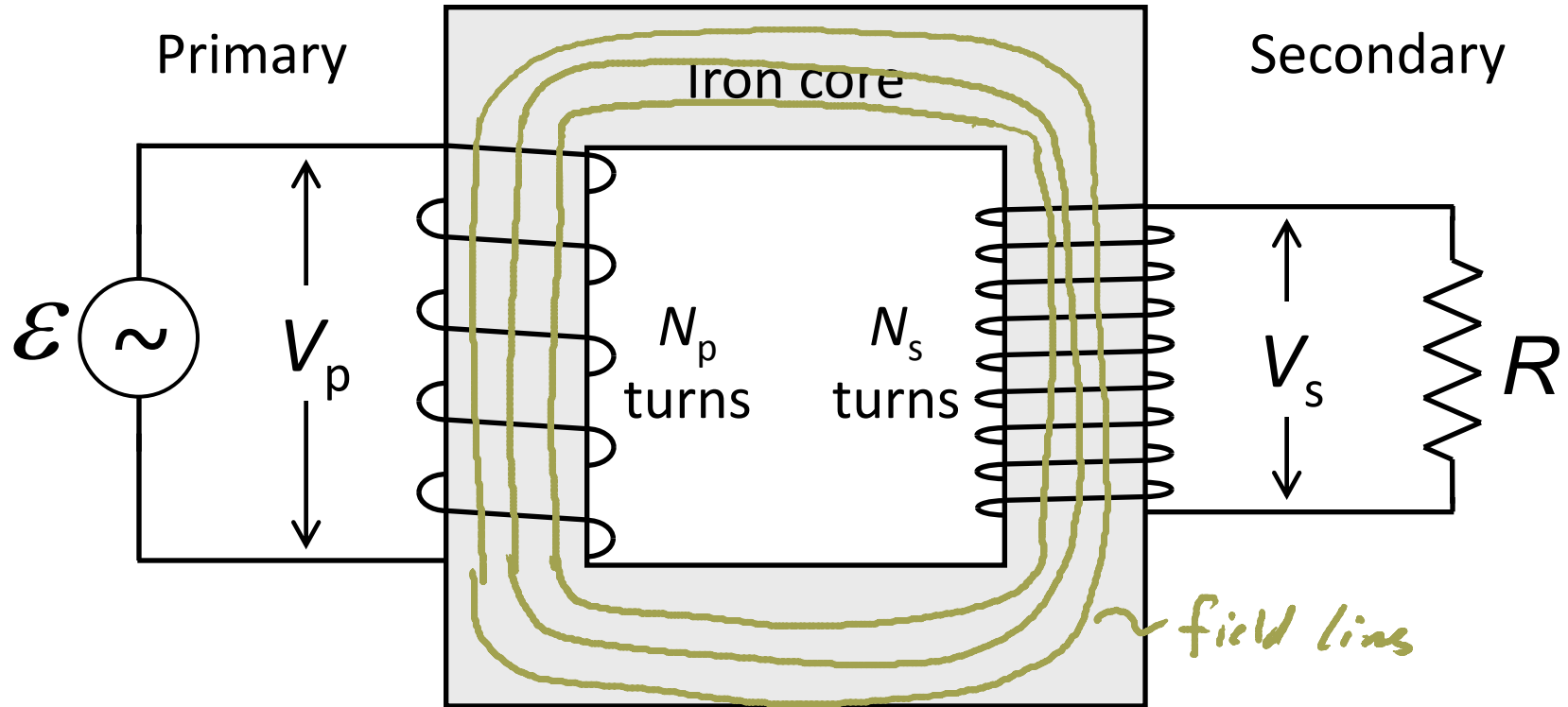

The iron core ensures that the Φ_B per turn is the same in both the primary & secondary windings.

$$\oint_{B, \text{Primary}} \Phi_B = \oint_{B, \text{Secondary}} \Phi_B \Rightarrow \frac{d\Phi_{B, \text{Pr}}}{dt} = \frac{d\Phi_{B, \text{Sec}}}{dt}$$

Transformer:

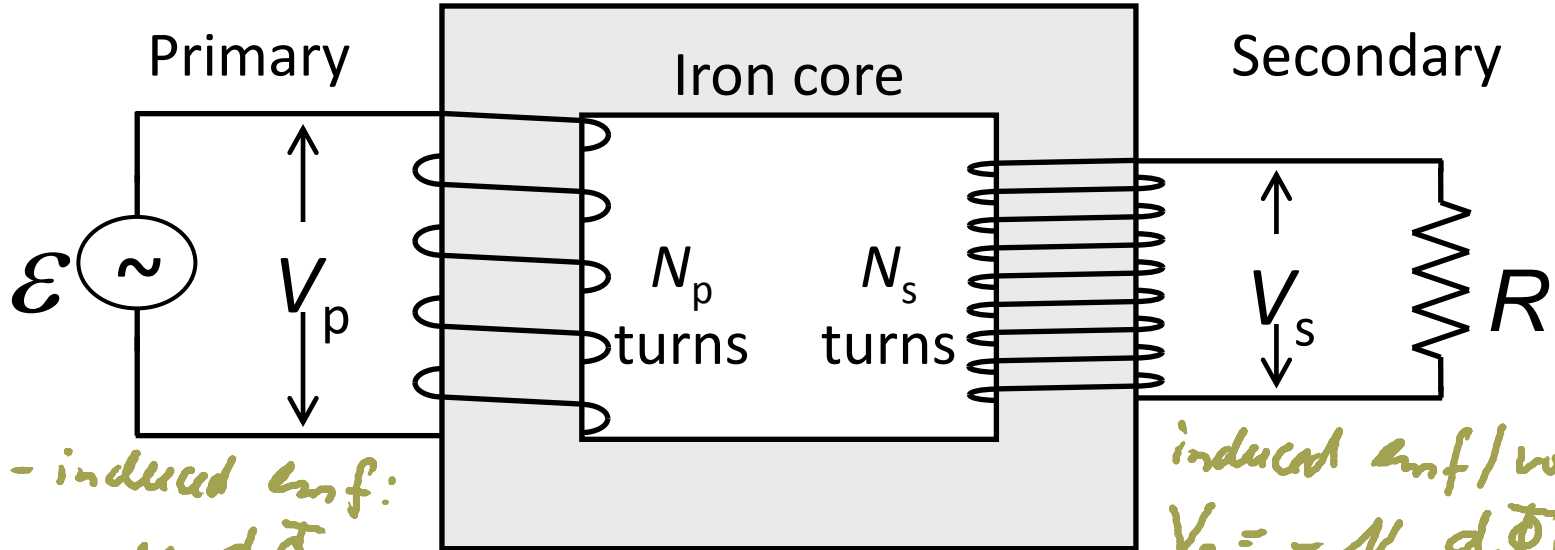

Self-induced emf:

$$V_p = -N_p \frac{d\Phi_B}{dt}$$

$$\Rightarrow \frac{V_s}{V_p} = \frac{N_s}{N_p} \frac{d\Phi_B/dt}{d\Phi_B/dt} = \frac{N_s}{N_p}$$

\Rightarrow Conservation of energy requires:
 $P_{in} = i_p V_p = P_{out} = i_s V_s$

$$\Rightarrow \underline{i_s} = i_p \frac{V_p}{V_s} = i_p \frac{N_p}{N_s}$$

ratio of turns determines output voltage V_s

- if $N_s > N_p$: step-up transformer
- if $N_s < N_p$: step-down transformer

Ideal LC – circuit (no resistance)

Energy stored in the electric field of capacitor


$$U_E = \frac{1}{2} \frac{q^2}{C}$$

=> Total energy stored:

$$U_{\text{total}} = U_E + U_B = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} L i^2 = \text{const}$$

Energy stored in the magnetic field of the inductor


$$U_B = \frac{1}{2} L i^2$$

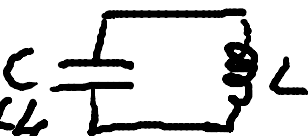

- Energy is conserved, so this total sum is constant, if there is no resistance in the circuit!
- But: energy can oscillate back and forth between electric field energy in the capacitor and magnetic field energy in the inductor!

Electromagnetic Oscillations in ideal LC circuit:

Capacitor starts with charge $q = Q$

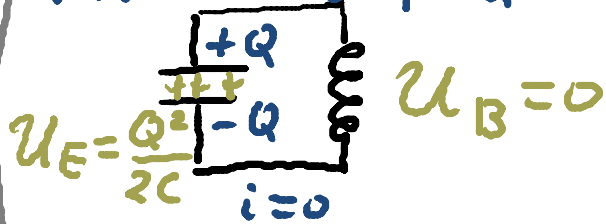

all energy is in the electric field


L tries to keep the current going, so C charges up again

Current starts to flow and C discharges

L regulates the increase in current

Circuit oscillates!


Current increases until $q = 0$

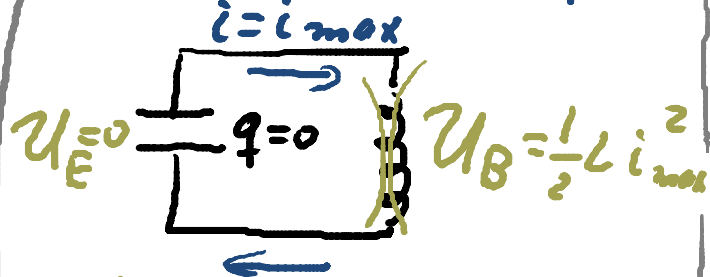

all energy is in the magnetic field

L tries to keep the current going, so C gets charged again, but with opposite polarity

Current increases until $q = 0$

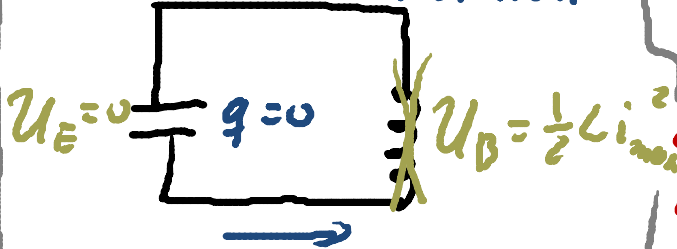


all energy is in the magnetic field


Current starts to flow and C discharges

L regulates the increase in current

Current decreases to $i = 0$

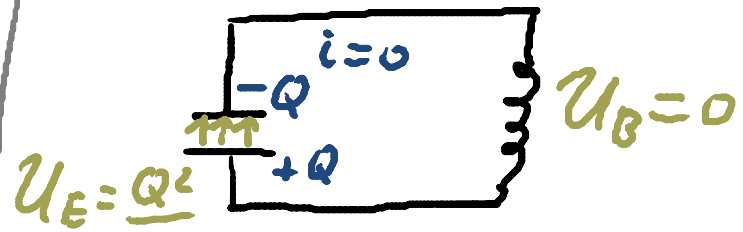

all energy is in the electric field

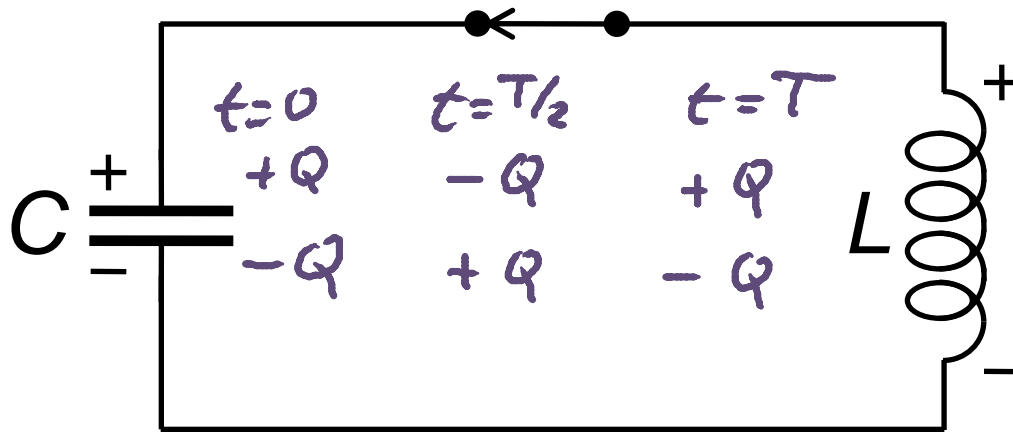

The capacitor starts with charge Q . At time $t = 0$ the switch is closed. Let T represent the period of the circuit oscillations.


What is the charge on the capacitor at time $T/2$?

- A. 0 B. $+Q/2$ C. $-Q/2$ D. $+Q$ E. $-Q$

Ideal LC-circuit (no resistance):

$$i = \frac{dq}{dt} < 0$$

q = charge on capacitor

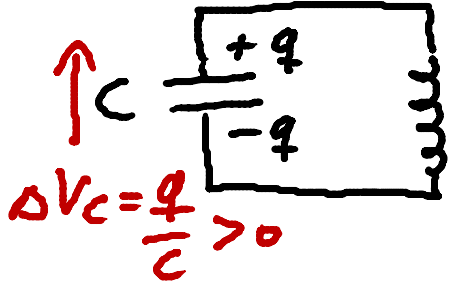

$$\Delta V_L = L \frac{di}{dt} = L \frac{d}{dt} \frac{dq}{dt} = L \frac{d^2 q}{dt^2} < 0$$

since $i = \frac{dq}{dt}$

2nd derivative wrt time

\Rightarrow loop rule gives: $\Delta V_C + \Delta V_L = 0$

$\Rightarrow \frac{q}{C} + L \frac{d^2 q}{dt^2} = 0$ } differential equation for oscillation of charge q in LC circuit

Solution:

$\phi = 0$


$q(t) = Q \cos(\omega t + \phi)$ } same oscillations as in SHM!

max. charge on capacitor during oscillation



⇒ current in LC circuit:
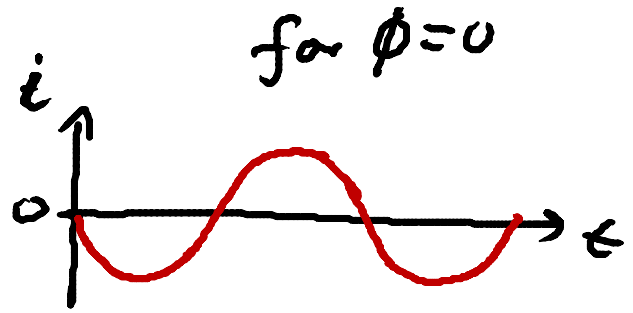
$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$



⇒ find angular frequency ω of oscillation:

need: $\frac{d^2q}{dt^2} = \frac{di}{dt} = -\omega^2 Q \cos(\omega t + \phi)$

insert into differential equation: $\frac{q}{C} + L \frac{d^2q}{dt^2} = 0$

$$\frac{Q}{C} \cos(\omega t + \phi) - L \omega^2 Q \cos(\omega t + \phi) = 0$$

gives: $\frac{1}{C} - L \omega^2 = 0 \Rightarrow$

$$\omega_{0,LC} = \frac{1}{\sqrt{LC}}$$

natural angular frequency for LC-circuit without damping

⇒ total energy in LC oscillator:

$$\begin{aligned}U_{\text{total}} &= U_E + U_B = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} L i^2 \quad \omega^2 = \frac{1}{LC} \\&= \frac{1}{2} \frac{Q^2}{C} \cos^2(\omega t + \phi) + \frac{1}{2} L \omega^2 Q^2 \sin^2(\omega t + \phi) \\&= \frac{1}{2} \frac{Q^2}{C} \underbrace{(\cos^2(\omega t + \phi) + \sin^2(\omega t + \phi))}_{=1} \\&= \frac{1}{2} \frac{Q^2}{C} = U_{E, \text{max}} = U_{B, \text{max}} = \underline{\underline{\text{const}}}\end{aligned}$$

⇒ Energy oscillates between electric and magnetic fields, but the total sum remains constant!

(like for SHM of a mass on a spring: energy oscillates between kinetic and potential energy)